
Logic and Computer Design Fundamentals

Chapter 3 – Combinational Logic Design

Part 1 – Implementation Technology and Logic Design

Asst.Prof.Dr. Preecha Tangworakitthaworn
Semester 2/2023

Overview

- **Part 1**

What is Combinational Circuits?


Design Procedure

- **Steps**

- **Specification**
- **Formulation**
- **Optimization**
- **Technology Mapping**
- **Verification**

Combinational Circuits

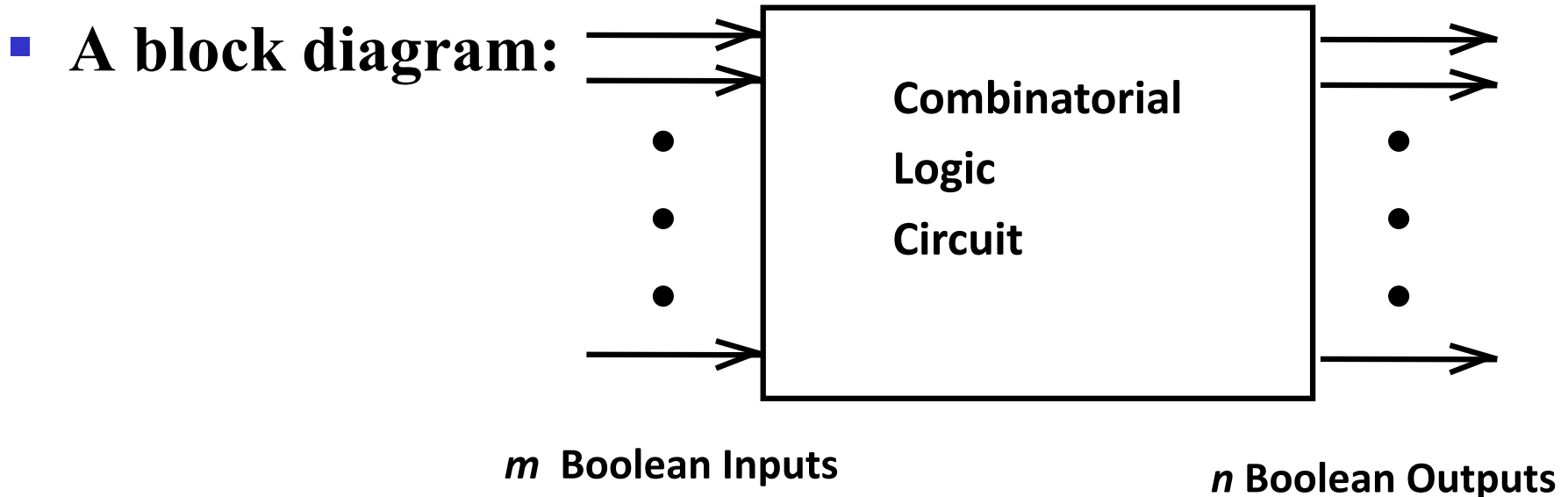- A combinational logic circuit has:
 - A set of m Boolean inputs,
 - A set of n Boolean outputs, and
 - n switching functions, each mapping the 2^m input combinations to an output such that the current output depends only on the current input values



Design Procedure

1. Specification

- Write a specification for the circuit if one is not already available

2. Formulation

- Derive a truth table or initial Boolean equations that define the required relationships between the inputs and outputs, if not in the specification

3. Optimization

- Optimize the expression until meets the smallest literals using K-Map technique

Design Procedure

4. Technology Mapping

- Draw a logic diagram for the resulting circuit using ANDs, ORs, and inverters

5. Verification (optional step)

- Verify the correctness of the final design manually or using simulation

Design Example

1. Specification

- **BCD to Excess-3 code converter**
- **Transforms BCD code for the decimal digits to Excess-3 code for the decimal digits**
- **BCD code words for digits 0 through 9: 4-bit patterns 0000 to 1001, respectively**
- **Excess-3 code words for digits 0 through 9: 4-bit patterns consisting of 3 (binary 0011) added to each BCD code word**
- **Implementation:**
 - **multiple-level circuit**
 - **NAND gates (including inverters)**

Design Example (continued)

2. Formulation

- Conversion of 4-bit codes can be most easily formulated by a truth table

- Variables

- BCD:

A,B,C,D

- Variables

- Excess-3

W,X,Y,Z

- Don't Cares

- BCD 1010

to 1111

Input BCD A B C D	Output Excess-3 W X Y Z
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0

Design Example (continued)

3. Optimization^z





a. 2-level using K-maps

$$W = A + BC + BD$$

$$X = \bar{B}C + \bar{B}D + B\bar{C}\bar{D}$$

$$Y = CD + \bar{C}\bar{D}$$


$$Z = \bar{D}$$

    

Design Example (continued)

4. Technology Mapping

- **Mapping to a final logic diagram**

 

2nd Example

Design of a BCD-to-Seven-Segment Decoder





Sample:

<https://www.youtube.com/watch?v=dS7VLZwz6bY>


<https://www.youtube.com/watch?v=-aCqfE2330w>

Design Procedure

Step 1 Specification

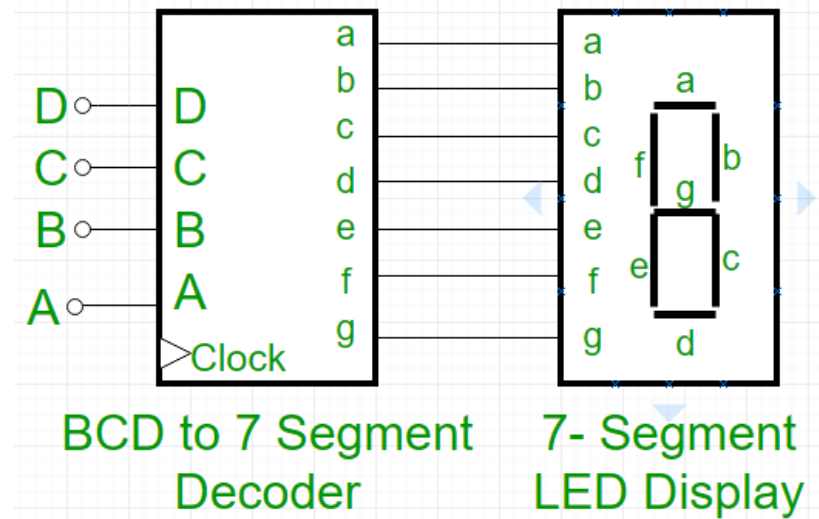 

1.1 Segment Designation

 

1.2 Display LED Designation

Design Procedure








Step 2 Formulation (Truth table)

Method 1
Without
“Don’t care”

Input					Output						
Dec	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
All other inputs					0	0	0	0	0	0	0

Design Procedure

Step 3 Optimization (K-Map)

       

Design Procedure

Step 3 Optimization (results Boolean functions)

$$a = \overline{A}C + \overline{A}\overline{B}\overline{D} + \overline{A}BD + A\overline{B}\overline{C}$$

$$b = \overline{A}\overline{B} + \overline{B}\overline{C} + \overline{A}\overline{C}\overline{D} + \overline{A}CD$$

$$c = \overline{A}B + \overline{B}\overline{C} + \overline{A}D$$

$$d = \overline{A}B\overline{C}D + A\overline{B}\overline{C} + \overline{A}\overline{B}\overline{D} + \overline{A}\overline{B}C + \overline{A}C\overline{D}$$

$$e = \overline{B}\overline{C}\overline{D} + \overline{A}C\overline{D}$$

$$f = A\overline{B}\overline{C} + \overline{A}B\overline{D} + \overline{A}B\overline{C} + \overline{A}\overline{C}\overline{D}$$

$$g = A\overline{B}\overline{C} + \overline{A}B\overline{C} + \overline{A}\overline{B}C + \overline{A}C\overline{D}$$

Design Procedure

Step 4 Technology Mapping (Logic Diagram)

refer to your solution of “In-class Activity 9”

Design Procedure

Step 2 Formulation (Truth table)


Method 2
With
“Don’t care”

Dec	Input				Output						
	A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1
All other inputs					X	X	X	X	X	X	X


Design Procedure

Step 3 Optimization (K-Map)

Output “a”

 


Output “b”

 


Design Procedure


Output “c” C

 


Output “d” C

 

Output “e” C

 

Output “f” C

 

Design Procedure

Output “g”

C

A

0	0	1	1
1	1	0	1
X	X	X	X
1	1	X	X

D

B

$$a = A + C + BD + \bar{B} \bar{D}$$

$$b = \bar{B} + \bar{C} \bar{D} + CD$$

$$c = B + \bar{C} + D$$

$$d = \bar{B} \bar{D} + C \bar{D} + B \bar{C} D + \bar{B} C + A$$

$$e = \bar{B} \bar{D} + C \bar{D}$$

$$f = A + \bar{C} \bar{D} + B \bar{C} + B \bar{D}$$

$$g = A + B \bar{C} + \bar{B} C + C \bar{D}$$

Design Procedure

Step 4 Technology Mapping (Logic Diagram)

