
Logic and Computer Design Fundamentals

Chapter 2 – Combinational Logic Circuits


Part 1 – Gate Circuits and Boolean Equations

Overview

- **Part 1 – Gate Circuits and Boolean Equations**
 - **Binary Logic**
 - **Logic Gates**
 - **Boolean Algebra**

I. Binary Logic

Logic

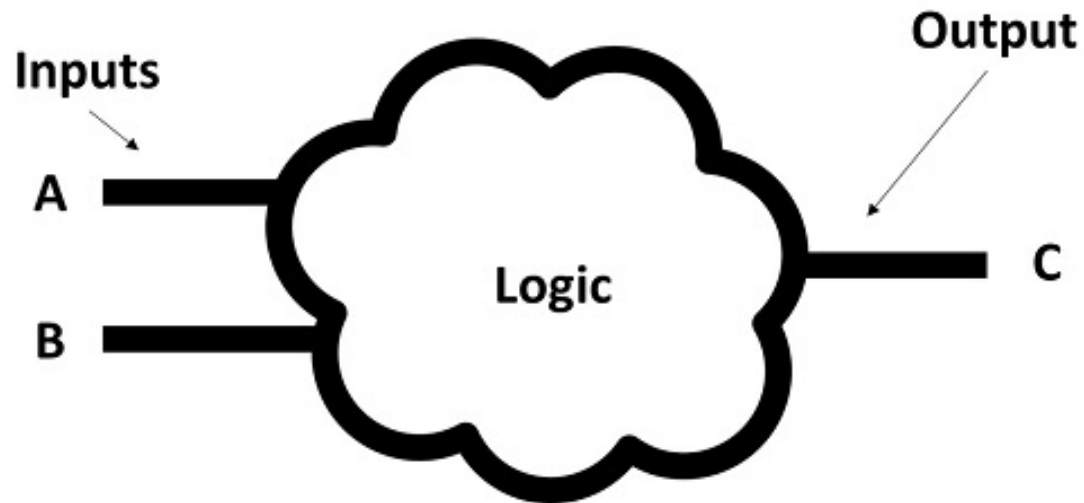

Binary Logic and Gates

- Binary variables take on one of two values.
- Logical operators operate on binary values and binary variables.
- Basic logical operators are the logic functions AND, OR and NOT.
- Logic gates implement logic functions.
- Boolean Algebra: a useful mathematical system for specifying and transforming logic functions.
- We study Boolean algebra as a foundation for designing and analyzing digital systems!

Binary Variables


- Recall that the two binary values have different names:
 - True/False
 - On/Off
 - Yes/No
 - 1/0
- We use 1 and 0 to denote the two values.
- Variable identifier examples:
 - A, B, x, y, or X_1 for now
 - RESET, START_IT, or ADD1 later

Logic Function Implementation


■ Using Switches

- For inputs:
 - logic 1 is switch closed
 - logic 0 is switch open
- For outputs:
 - logic 1 is light on
 - logic 0 is light off.

Switches in parallel => OR

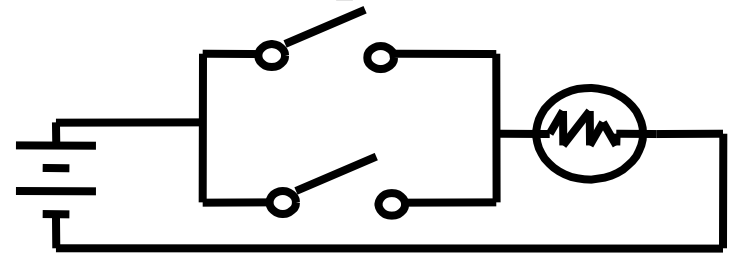

Switches in series => AND

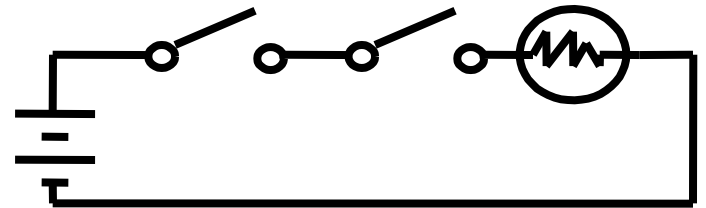

Logical Operations

- The three basic logical operations are:
 - AND
 - OR
 - NOT
- AND is denoted by a dot (\cdot).
- OR is denoted by a plus ($+$).
- NOT is denoted by an overbar ($\bar{}$), a single quote mark ($'$) after, or dash (\sim) before the variable.

Notation Examples

- Examples:

- $Y = A \cdot B$ is read “Y is equal to A AND B”
- $a = x + y$ is read “a is equal to x OR y”
- $X = \bar{A}$ is read “X is equal to NOT A”

the reduced form of AND is $Y = AB$

- Note: The statement:

$1 + 1 = 2$ (read “one plus one equals two”)

is not the same as

$1 + 1 = 1$ (read “1 or 1 equals 1”)

Operator Definitions

Operations are defined on the values "0" and "1" for each operator:

AND

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

NOT

$$\bar{0} = 1$$

$$\bar{1} = 0$$

Boolean Operator Precedence

- The order of evaluation in a Boolean expression is:
 1. Parentheses
 2. NOT
 3. AND
 4. OR
- Consequence: Parentheses appear around OR expressions
- Example: $F = A(B + C)(C + \overline{D})$

Truth Tables

- *Truth table* – a tabular listing of the values of a function for all possible combinations of values on its arguments
- Example: Truth tables for the basic logic operations:

AND		
X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR		
X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT	
X	$Z = \bar{X}$
0	1
1	0


Practice: Q1

Complete the following truth table:

A	B	C	$A \cdot B \cdot C$	$\overline{A} + (B \cdot C)$	$(A + B) \cdot \overline{C}$
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

II. Logic Gates

Logic Gates



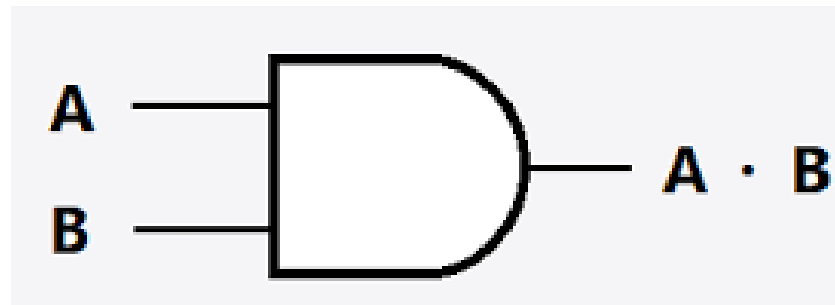


Logic Gates

- A logic gate is an idealized model of computation or physical electronic device implementing the Boolean function, a logical operation performed on one or more binary inputs that produces a single binary output.


Logic Gate Symbols and Behavior

Three basic symbols for Logic gates:

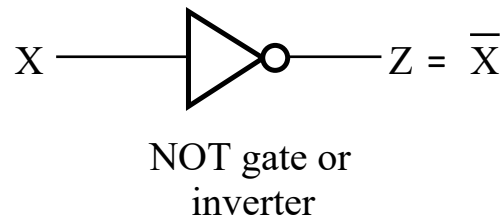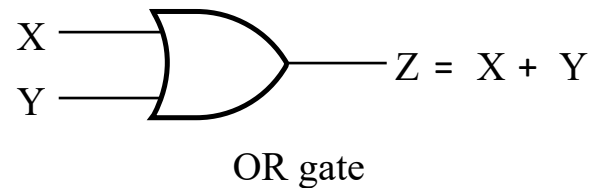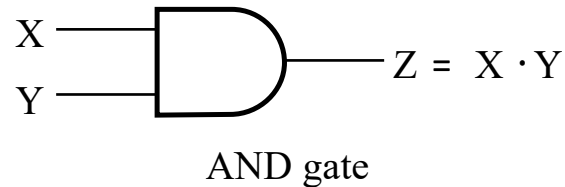

Timing Diagram

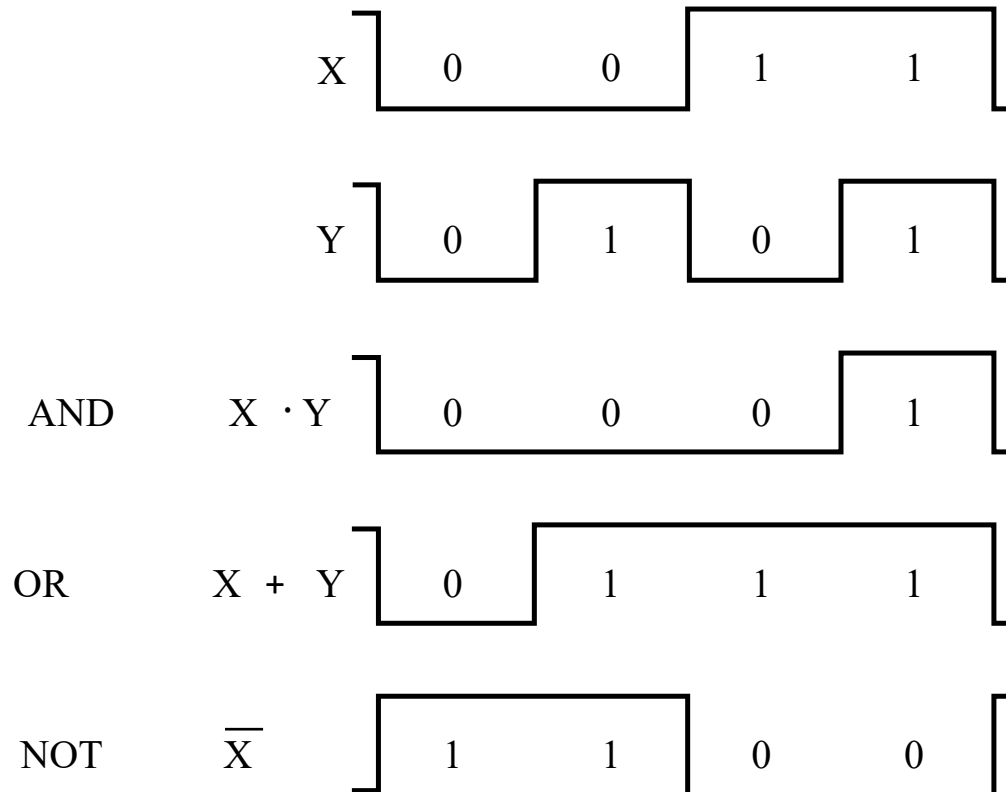Timing Diagram represents the waveform behavior in time as follows



Logic Diagram

- Logic diagram is a diagram that displays graphically, by interconnection of logic symbols, the digital design of a logic circuit or system.

Logic Diagrams and Expressions


Truth Table

X Y Z	$F = X + \bar{Y} \cdot Z$
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	1

Equation

$$F = X + \bar{Y} Z$$

Logic Diagram

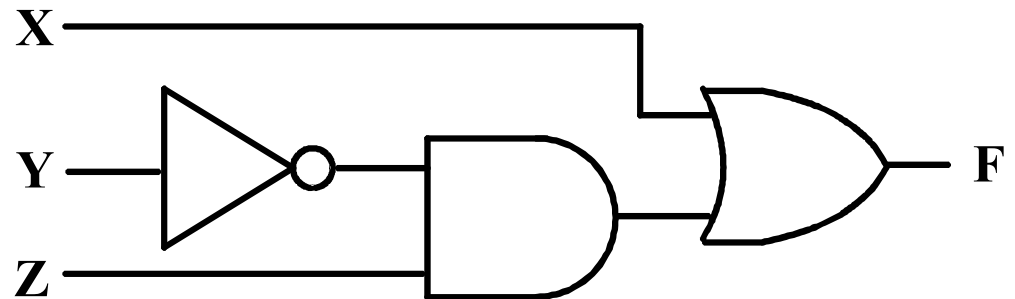

- Boolean equations, truth tables and logic diagrams describe the same function