
Logic and Computer Design Fundamentals

Chapter 2 – Combinational Logic Circuits

Part 2 – Additional Gates and Circuits

Asst.Prof.Dr. Preecha Tangworakitthaworn
Semester 2/2023

Overview

- **Part 1 – Review Basic Logic Gates and Behavior**
- **Part 2 – Additional Gates and Circuits**
 - **Other Gate Types**
 - **Exclusive-OR Operator and Gates**




Part 1 – Review Basic Logic Gates

What is the logic gate?



A logic gate is a device performing a Boolean Logic Operation on one or more binary inputs and then give a single binary output.

Part 1 – Review Basic Logic Gates

Three basic symbols for Logic gates:

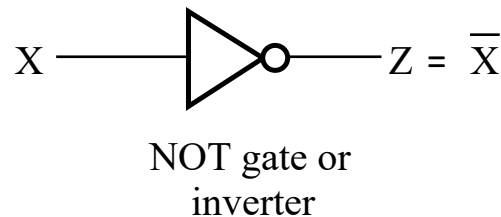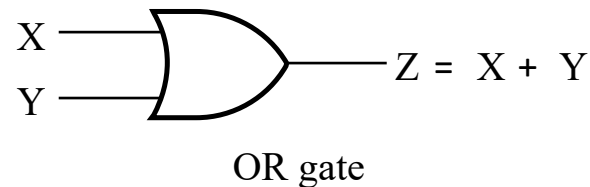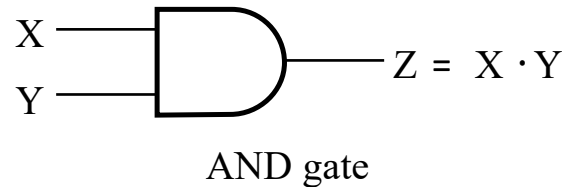

Basic Logic Gates formation

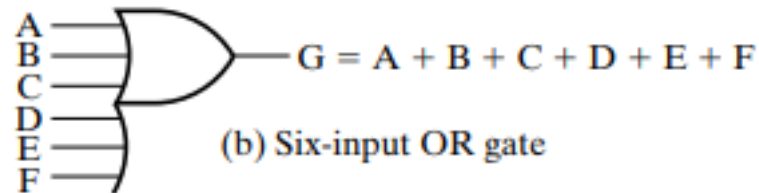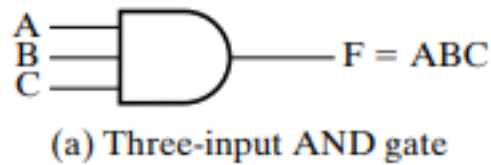

A single-output Boolean function is a mapping from each of the possible combinations of input values 0 and 1 on the function variables to output value 0 or 1.

Behavior and Representation

- **Truth table** is a representation of gates' behavior described its basic logic operations:

AND		
X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR		
X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

NOT	
X	$Z = \overline{X}$
0	1
1	0

Behavior and Representation

- **Truth table** for more variables can be listed the combination as follows:

2 Variables = 2^2

	A	B
0	0	0
1	0	1
2	1	0
3	1	1

4 combinations

3 Variables = 2^3

	A	B	C
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

8 combinations

4 Variables = 2^4

	A	B	C	D
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
.	0	0	1	1
.	0	1	0	0
	0	1	0	1
	0	1	1	0
	0	1	1	1

16 combinations


	A	B	C	D
	1	0	0	0
	1	0	0	1
	1	0	1	0
	1	0	1	1
	1	1	0	0
	1	1	0	1
	1	1	1	0
	1	1	1	1

14

15


Behavior and Representation

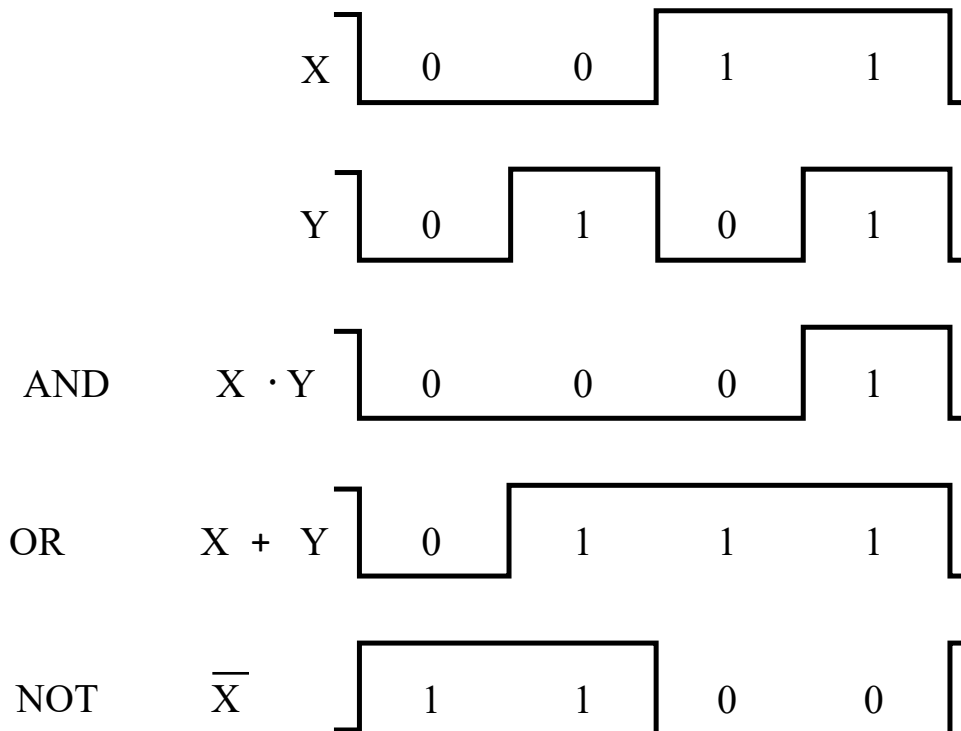- **Timing Diagram** is a representation of gates' behavior described its logic operations based on Time:



Behavior and Representation

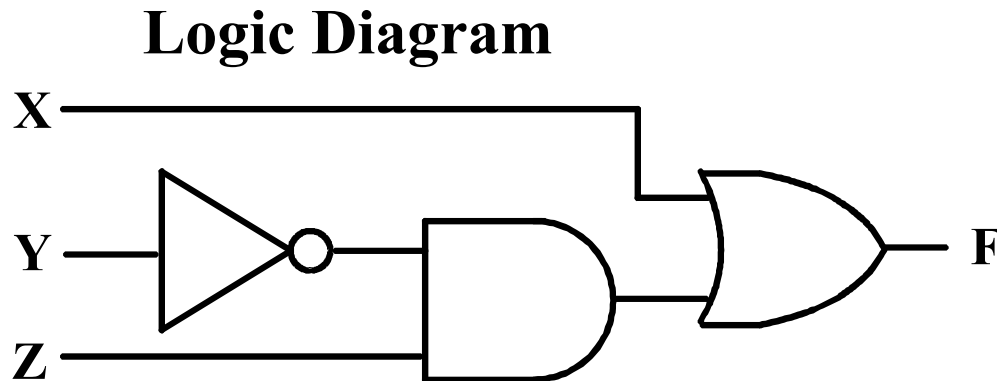
- **Logic Diagram (or Circuit Diagram)**
consists of gates and symbols that can directly replace an expression in Boolean function or Boolean equation:



Boolean Equation


$$F = X + \overline{Y} Z$$

Example of Circuit Diagram

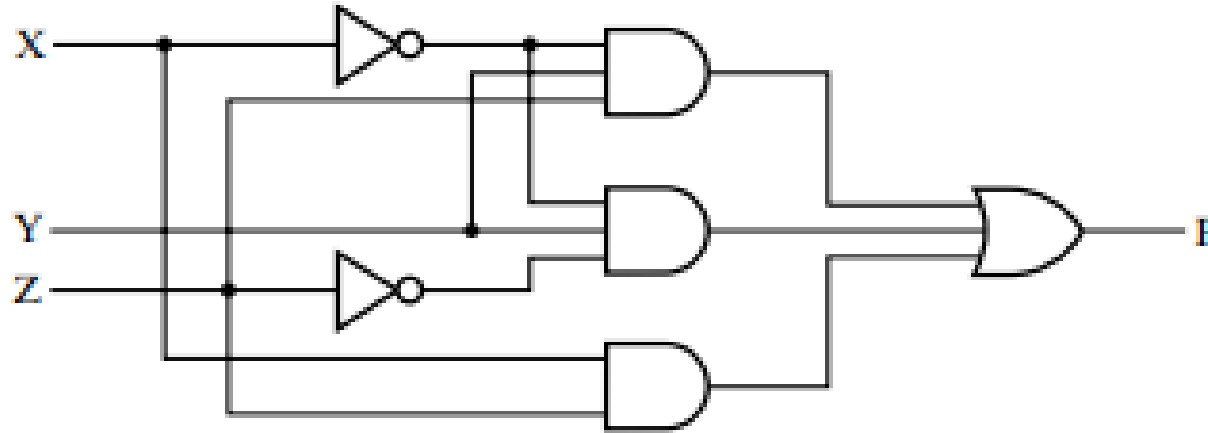

$$F(X,Y,Z) = \bar{X}YZ + \bar{X}Y\bar{Z} + XZ$$

Example of Circuit Diagram

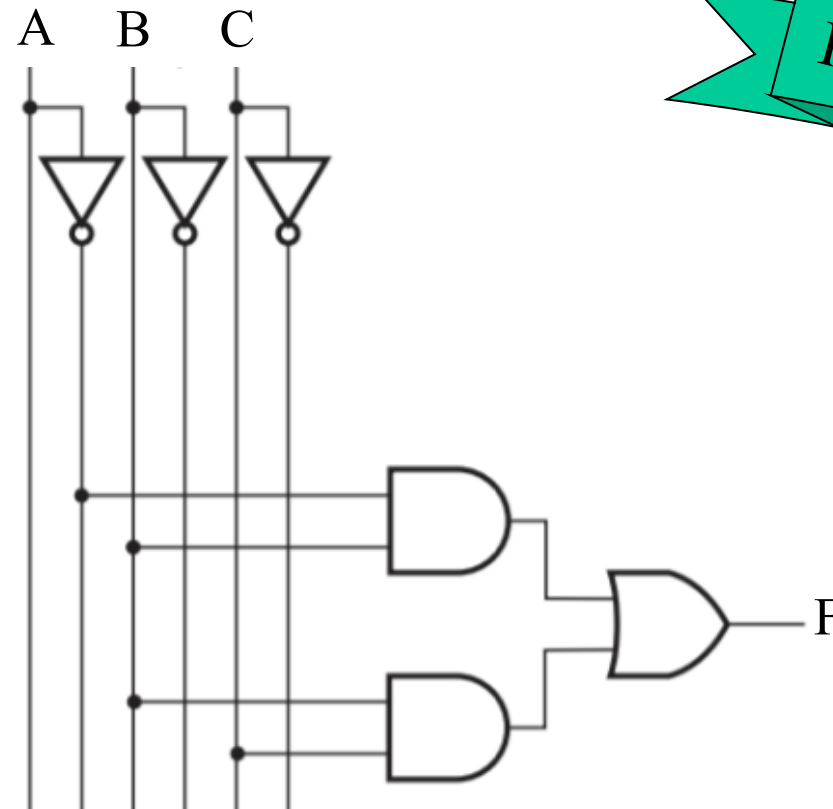

Recommend

$$F(A,B,C) = \bar{A}B + BC$$

Software for Drawing [online]

- [**https://www.circuitlab.com/**](https://www.circuitlab.com/)
- [**https://cloud.smartdraw.com/**](https://cloud.smartdraw.com/)
- [**https://www.digikey.it/schemeit/project/**](https://www.digikey.it/schemeit/project/)


Part 2 – Other Gate Types

- Why?
 - Implementation feasibility and low cost
 - Power in implementing Boolean functions
 - Convenient conceptual representation
- Gate classifications
 - Primitive (or basic) gate - a gate that can be described using a single primitive operation type (AND or OR) plus an optional inversion (NOT).
 - Complex gate - a gate that requires more than one primitive operation type for its description.

NAND Gate

Recommend

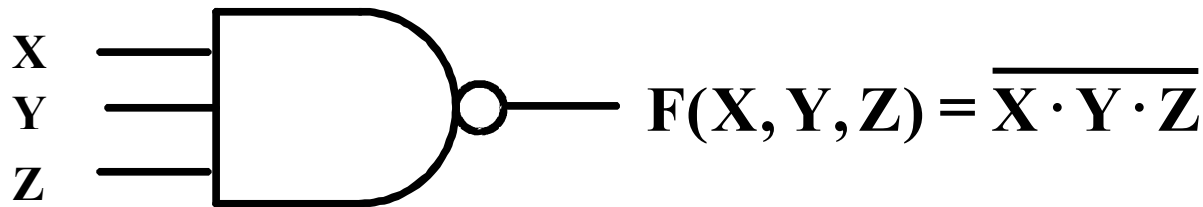
- The basic NAND gate has the following symbol, illustrated for three inputs:
 - AND-Invert (NAND)




- NAND represents NOT AND, i. e., the AND function with a NOT applied. The symbol shown is an AND-Invert. The small circle (“bubble”) represents the invert function.

NAND Gate (continued)

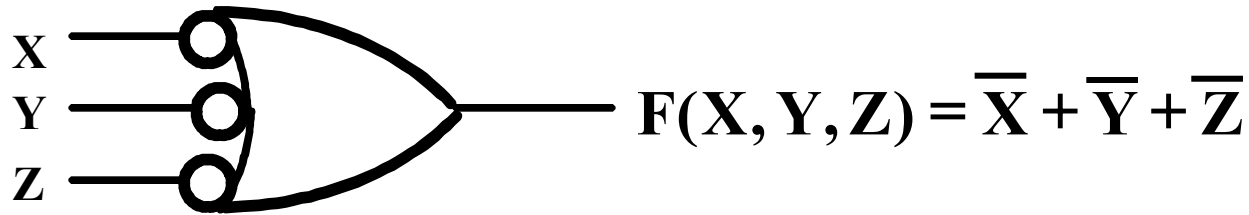- Applying DeMorgan's Law gives Invert-OR (NAND)



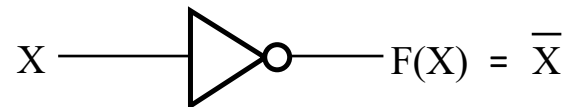- This NAND symbol is called **Invert-OR**, since inputs are inverted and then operate OR together.
- AND-Invert and Invert-OR both represent the NAND gate. Having both makes visualization of circuit function easier.
- A NAND gate with one input degenerates to an inverter.




NOR Gate

Recommend

- The basic NOR gate has the following symbol, illustrated for three inputs:


- OR-Invert (NOR)

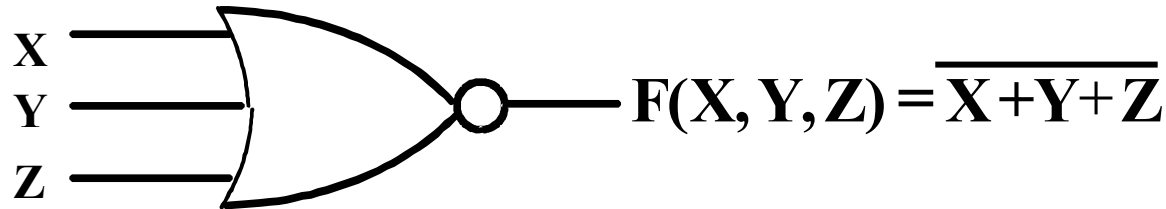

- NOR represents NOT - OR, i. e., the OR function with a NOT applied. The symbol shown is an OR-Invert. The small circle (“bubble”) represents the invert function.

NOR Gate (continued)

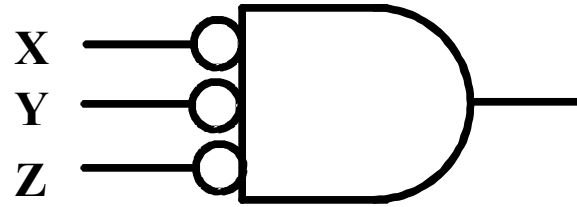- Applying DeMorgan's Law gives Invert-AND (NOR)



- This NOR symbol is called **Invert-AND**, since inputs are inverted and then operate AND together.
- OR-Invert and Invert-AND both represent the NOR gate. Having both makes visualization of circuit function easier.
- A NOR gate with one input degenerates to an inverter.

Exclusive OR/ Exclusive NOR

- The *eXclusive OR (XOR)* function is an important Boolean function used extensively in logic circuits.
- The *eXclusive NOR (XNOR)* function is the complement of the XOR function.
- By definition, XOR and XNOR gates are complex gates.

Exclusive OR/ Exclusive NOR



Recommend

■ Definitions

- The XOR function is:

$$X \oplus Y = X \bar{Y} + \bar{X} Y$$

- The eXclusive NOR (XNOR) function, otherwise known as *equivalence* is:

$$\overline{X \oplus Y} = XY + \bar{X} \bar{Y}$$

Truth Tables for XOR/XNOR

- Operator Rules: XOR

X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

- XNOR

X	Y	$\overline{(X \oplus Y)}$
0	0	1
0	1	0
1	0	0
1	1	1

- The XOR function means:
X OR Y, but NOT BOTH

XOR/XNOR

The XOR function can be extended to 3 or more variables. Processing step by step will help you to not confuse!

A	B	$A \oplus B$	C	$(A \oplus B) \oplus C$
0	0	0	0	0
0	0	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1

XOR/XNOR (Continued)

Recommend

- The XOR function can be extended to 3 or more variables. For more than 2 variables, it is called an *odd function* or *modulo 2 sum (Mod 2 sum)*, not an XOR:

$$X \oplus Y \oplus Z = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$

- The complement of the odd function is the even function.
- The XOR identities:

$$X \oplus 0 = X$$

$$X \oplus X = 0$$

$$X \oplus Y = Y \oplus X$$


$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z$$

$$X \oplus 1 = \bar{X}$$


$$X \oplus \bar{X} = 1$$

Symbols For XOR and XNOR


- **XOR symbol:**

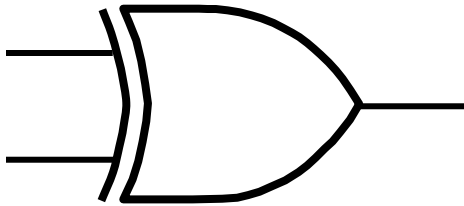


- **XNOR symbol:**

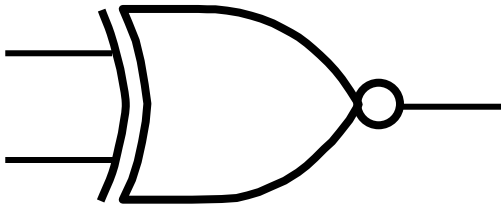

XOR Implementations

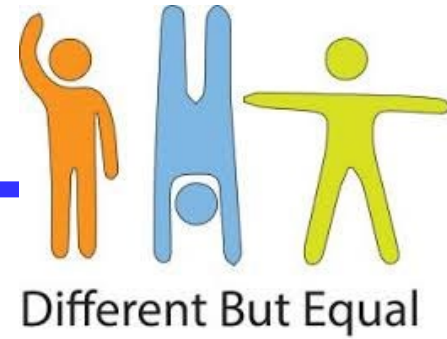

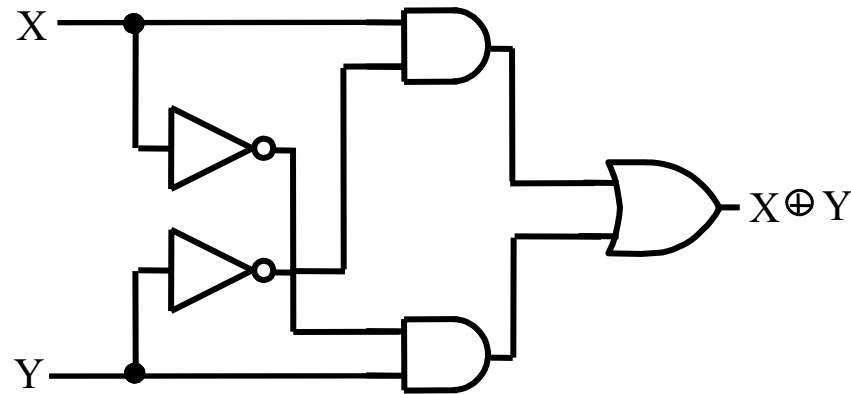The simple implementation uses the following structure:



which is equivalent to.. XOR gate implementation:

